# Secondary wiring of the head unit

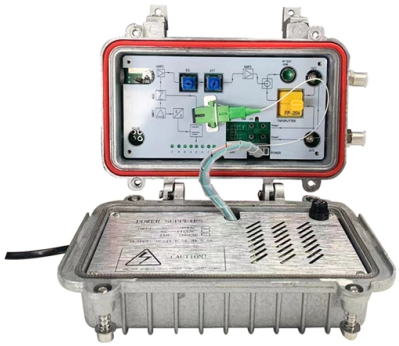

## Overview

Learn about aftermarket head unit wiring harnesses and how they can help you install a new car stereo in your vehicle.

## Key Takeaways

Secondary wiring involves connecting auxiliary features like reverse camera triggers, steering wheel controls, amplifier turn-on, and antenna power to ensure full functionality of your head unit.Key Secondary Connections

1. Reverse Trigger and Brake Wires These wires activate features such as a reverse camera or parking sensors when the vehicle is in reverse. Typically, the reverse trigger wire is connected to the vehicle's reverse light circuit, sending a 12V signal to the head unit to switch the display automatically when reversing . 2. Steering Wheel Control (SWC) Wires SWC wires allow the head unit to interface with factory steering wheel buttons. These often require a CAN bus adapter or a dedicated SWC interface module to translate button presses into commands the aftermarket head unit can recognize . 3. Antenna and Amplifier Power

• Antenna power wire provides 12V to power a powered antenna or antenna amplifier.

© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved

• Amplifier remote turn-on wire sends a 12V signal from the head unit to external amplifiers, ensuring they power on only when the stereo is active . 4. Factory Reverse Camera Integration Some vehicles have factory cameras that can be connected to aftermarket head units. This usually involves tapping into the factory video signal and reverse trigger wire, often requiring a specific adapter for compatibility . 5. CAN Bus and Modern Vehicle Integration Modern vehicles use CAN bus systems to communicate between modules. Secondary wiring may involve connecting the head unit to the CAN bus via an interface module to retain features like vehicle settings, warning chimes, and climate display integration .
Best Practices for Secondary Wiring
• Use a wiring harness adapter whenever possible to avoid cutting factory wires, preserving resale value and simplifying future upgrades .

• Label all wires before disconnecting to prevent misconnection.

• Test connections with a multimeter before final assembly to ensure proper voltage and continuity .

• Secure connections using soldering, crimp connectors, or solder seal connectors to prevent loose or intermittent contacts .

• Disconnect the battery before starting any wiring to prevent shorts or damage to vehicle electronics .
Summary

Secondary wiring is essential for enabling all auxiliary features of a head unit, including reverse cameras, steering wheel controls, amplifier turn-on, and antenna power. Proper identification, secure connections, and the use of adapters or interface modules ensure reliable operation and integration with modern vehicle systems .

## Article Content

Head Unit Installation: Wire Colors & Steps | Audio

Complete head unit installation guide. Correct wire colors (Yellow=Constant, Red=Switched), harness

Aftermarket Head Unit Wiring Explained | What Every Wire Does

Confused by aftermarket head unit wiring? In this tutorial, we break down what every major wire and plug actually

Head Unit Wiring Guide and Connections

Learn how to correctly wire your head unit with this detailed guide. Find connection diagrams, tips, and step-by-step instructions for

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

How to Wire a Head Unit: A Step-by-Step Guide

Successfully installing a new head unit requires a precise understanding of automotive electrical connections and

Wiring the Head Unit: Simplified Diagram

Learn how to properly wire a car head unit using a wiring diagram. Get step-by-step instructions and tips

How to Wire an Amp to a Sub and Head Unit: DIY Guide

If you want to wire an amp to a sub and head unit, start by turning your vehicle off and

3 Easy Methods for Wiring Your Aftermarket Head Unit

In this article, I''ll walk you through through 3 common methods that are used to merge an

How hard is it to add a second head unit? : r/CarAV

I''m asking how hard it would be to tear all original speakers out and wire in a new system to a new headunit installed in a hidden

Complete Wiring Diagram for Head Unit & Motorized Accessories

This comprehensive motor wiring tutorial will walk you through the exact pinouts, relay integration, and flyback diode

Methods for Wiring Your Aftermarket Head Unit

In this video, we walk through 3 common methods merging an aftermarket head unit harness to a vehicle specific

baboombaboom

We would like to show you a description here but the site won''t allow us.

Aerpro | First Choice

Aerpro''s range of secondary harnesses will plug into any Aerpro Primary Harness including the Steering

A DIY Guide to Installing a New Head Unit

Explore this brief step-by-step guide, complete with images, on how to install a car stereo head unit.

How to Wire a Head Unit: A Step-by-Step Guide

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

The yellow wire supplies constant 12-volt power directly from the battery, maintaining memory settings such as radio

3 Easy Methods for Wiring Your Aftermarket Head Unit

Discover 3 easy methods for wiring your aftermarket head unit. Get done quickly with no

Car Head Unit Wiring Diagram

Moreover, if you are planning to upgrade your car''s audio system, a wiring diagram will make the installation process much smoother

How to HARDWIRE a Car Stereo / Head Unit without a Wiring ...

If your Stereo wiring is cut or there is no wiring harness available, you might have to do a

The Ultimate Guide to Installing an Aftermarket Head Unit: Everything ...

Learn about aftermarket head unit wiring harnesses and how they can help you install a new car stereo in your vehicle. Find out the

Installation Planning: Wiring Diagram for Kenwood Head Units

Master your car audio install with our planning guide to the wiring diagram for Kenwood head units. Covers wire colors,

How to Install a Head Unit on a Stereo

If you are not sure about the wiring, refer to a wiring diagram for guidance.

The Ultimate Car Audio Wiring Guide: How to Install and Upgrade

Learn how to properly wire your car audio system with this comprehensive guide. From connecting speakers to installing amplifiers,

Android Car Head Unit Wiring Diagram – Wiring Flow Schema

Android Car Head Unit Wiring Diagram: A Comprehensive Guide Do you own a car? Are you looking to upgrade your

Wiring Harnesses & Head Unit Adapters | Supercheap Auto

This integration allows your new head unit to easily align with your car''s existing wiring, eliminating the need for intricate

Aftermarket Stereo Wiring Harness Diagram Guide

Explore our comprehensive guide to aftermarket stereo wiring harness diagrams, helping you easily connect your car audio system

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

Home

Navitas acknowledges the Traditional Owners of the lands in Australia and respects all First Nations peoples in the countries in which

Aftermarket automotive Head units and Car Stereo pinouts

Aftermarket car audio devices The head unit is the centerpiece of the car sound system. Typically located in the center of the

How to Wire an Amp to a Sub and Head Unit: DIY Guide

If you want to wire an amp to a sub and head unit, start by turning your vehicle off and popping the hood. Next,

Connect My Headunit

Head Units 7 Modules 2 Headunit Upgrade Kits - Head Unit Included 334 Wireless Smartphone Monitors 15 Installation Kits 291

Head unit ground help. Read comments : r/CarAV

Top wire goes directly connected to the ground wire coming off factory plug behind head unit. No need to run directly to the battery. If

Aerpro | First Choice

Aerpro''s range of Secondary Harnesses with Patch Lead are designed to plug into any Primary Steering Wheel Control Adapter

baboombaboom

We would like to show you a description here but the site won''t allow us.

Aerpro | First Choice

Aerpro''s range of secondary harnesses will plug into any Aerpro Primary Harness including the Steering

A DIY Guide to Installing a New Head Unit

Explore this brief step-by-step guide, complete with images, on how to install a car stereo head unit.

How to Wire a Head Unit: A Step-by-Step Guide

The yellow wire supplies constant 12-volt power directly from the battery, maintaining memory settings such as radio

3 Easy Methods for Wiring Your Aftermarket Head Unit

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

Discover 3 easy methods for wiring your aftermarket head unit. Get done quickly with no

Car Head Unit Wiring Diagram

Moreover, if you are planning to upgrade your car''s audio system, a wiring diagram will make the installation process much smoother

How to Identify OEM Car Stereo Wires

OEM car radio wire colors vary widely from one car stereo to the next, but it''s actually pretty easy to identify what each

Car Head Unit Wiring Diagram

Furthermore, a wiring diagram also aids in the installation process of a new head unit. By following the diagram, one

Head Unit Installation: Wire Colors & Steps | Audio

Complete head unit installation guide. Correct wire colors (Yellow=Constant, Red=Switched), harness

How to Wire an Android Head Unit: Step-by-Step Wiring Diagram Guide

A precise wiring diagram is your roadmap to a safe, functional installation. This guide breaks down every wire,

How to HARDWIRE a Car Stereo / Head Unit without a Wiring ...

If your Stereo wiring is cut or there is no wiring harness available, you might have to do a hardwire install for your new

The Ultimate Guide to Installing an Aftermarket Head Unit: Everything ...

Learn about aftermarket head unit wiring harnesses and how they can help you install a new car stereo in your vehicle. Find out the

Installation Planning: Wiring Diagram for Kenwood Head Units

Master your car audio install with our planning guide to the wiring diagram for Kenwood head units. Covers wire colors,

How to Install a Head Unit on a Stereo

If you are not sure about the wiring, refer to a wiring diagram for guidance. When finished, the two harnesses should

Head Unit Installation: Wire Colors & Steps | Audio

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

Complete head unit installation guide. Correct wire colors (Yellow=Constant, Red=Switched), harness

Aftermarket Head Unit Wiring Explained | What Every Wire Does

Confused by aftermarket head unit wiring? In this tutorial, we break down what every major wire and plug actually

Head Unit Wiring Guide and Connections

Learn how to correctly wire your head unit with this detailed guide. Find connection diagrams, tips, and step-by-step instructions for

How to Wire a Head Unit: A Step-by-Step Guide

Successfully installing a new head unit requires a precise understanding of automotive electrical connections and

Wiring the Head Unit: Simplified Diagram

Learn how to properly wire a car head unit using a wiring diagram. Get step-by-step instructions and tips

How to Wire an Amp to a Sub and Head Unit: DIY Guide

If you want to wire an amp to a sub and head unit, start by turning your vehicle off and

3 Easy Methods for Wiring Your Aftermarket Head Unit

In this article, I''ll walk you through through 3 common methods that are used to merge an

How hard is it to add a second head unit? : r/CarAV

I''m asking how hard it would be to tear all original speakers out and wire in a new system to a new headunit installed in a hidden

Complete Wiring Diagram for Head Unit & Motorized Accessories

This comprehensive motor wiring tutorial will walk you through the exact pinouts, relay integration, and flyback diode

Methods for Wiring Your Aftermarket Head Unit

In this video, we walk through 3 common methods merging an aftermarket head unit harness to a vehicle specific

Head Unit Installation: Wire Colors & Steps | Audio

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*

Complete head unit installation guide. Correct wire colors (Yellow=Constant, Red=Switched), harness

Aftermarket Head Unit Wiring Explained | What Every Wire Does

Confused by aftermarket head unit wiring? In this tutorial, we break down what every major wire and plug actually

Head Unit Wiring Guide and Connections

Learn how to correctly wire your head unit with this detailed guide. Find connection diagrams, tips, and step-by-step instructions for

How to Wire a Head Unit: A Step-by-Step Guide

Successfully installing a new head unit requires a precise understanding of automotive electrical connections and

Wiring the Head Unit: Simplified Diagram

Learn how to properly wire a car head unit using a wiring diagram. Get step-by-step instructions and tips

How to Wire an Amp to a Sub and Head Unit: DIY Guide

If you want to wire an amp to a sub and head unit, start by turning your vehicle off and

Related Video Reference

This video was associated with the source search result. Verify technical details against current product documentation and project requirements.

## Contact Us

Continue your research online:

Website: https://alfa-pro.co.za
Technical inquiry: https://alfa-pro.co.za/contact.html

This document is for preliminary research. Verify specifications against current standards, product documentation and project requirements.

*© 2026 ALFA PRO COMMUNICATION SYSTEMS (Pty) Ltd - All rights reserved*